

lab 02

Process

Digital design – laboratory exercises

assistant: Nejc Ilc

Process

```
<label>: process (<sensitivity_list>)  
begin  
    -- statements - sequential order  
end
```

In `sensitivity_list` we put all signals that can cause changes in the outputs of the process.

"if" statement

- Use it only inside a process
- Syntax

```
if condition then
  -- statements
else
  -- statements
end if;
```

```
if condition_1 then
  -- statements
elsif condition_2 then
  -- statements
else
  -- statements
end if;
```


"case" statement

- Use it only inside a process
- Syntax

```
case s is
  when value_1 => output <= expression_1;
  when value_2 => output <= expression _2;
  ...
  when others => output <= expression _df1;
end case;
```

- Last case (`when others`) is mandatory.

Example

 

Using "case":

```
process (i, s)
begin
  case s is
    when "00" => o <= i(0);
    when "01" => o <= i(1);
    when "10" => o <= i(2);
    when "11" => o <= i(3);
    when others => o <= i(0);
  end case;
end process;
```

Using conditional assignment:

```
o <= i(0) when s="00" else
      i(1) when s="01" else
      i(2) when s="10" else
      i(3);
```

Using "select":

```
with s select
  o <= i(0) when "00",
      i(1) when "01",
      i(2) when "10",
      i(3);
```

Sequential circuits


- In sequential circuits, changes occur at clock events (at the first/positive/rising or last/negative/falling edge)
- We detect an event on a clock signal `clk` using `clk'event`
 - `clk'event` is `true`, when there is an edge on signal

- Rising edge detection

`clk'event and clk='1'`

- Falling edge detection

`clk'event and clk='0'`

 

Example: D flip-flop

```
process(clk)
begin
    if clk'event and clk = '1' then
        q <= d;
    end if;
end process;
```

Example: counter

```
process(clk)
begin
    if clk'event and clk = '1' then
        if reset = '1' then
            count <= (others => '0'); -- reset all bits on '0'
        else
            count <= count + 1;
        end if;
    end if;
end process;
```


Library IEEE: package STD_LOGIC_1164

- Package IEEE.STD_LOGIC_1164 defines (among others) types STD_LOGIC and STD_LOGIC_VECTOR and functions as:
 - rising_edge
instead of: clk'event and clk = '1'
 - falling_edge
instead of: clk'event and clk = '0'

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

Library IEEE: package NUMERIC_STD

```
use IEEE.NUMERIC_STD.all;
```

- Package IEEE.NUMERIC_STD defines types signed and unsigned and the corresponding arithmetic and logical operations on them:

`+, -, *`

`=, /=, <, <=, >, >=`

`shift_left(op1, op2), shift_right(op1, op2)`

- here, op1 is of type (un)signed and op2 is of type integer


Library IEEE: package NUMERIC_STD

Type conversion

- When using arithmetic operators, we often have to use type conversion, e.g.:
 - `std_logic_vector` \leftrightarrow signed/unsigned
 - `std_logic_vector` \leftrightarrow integer
 - `integer` \leftrightarrow signed/unsigned
- We use
 - casting, e.g.:
 - `unsigned(signal_std_logic_vector)`
 - `std_logic_vector(signal_unsigned)`
 - and conversion functions, e.g.:
 - `to_integer(signal_unsigned)`
 - `to_signed(signal_integer, bit_width)`
- Code examples: <https://nandland.com/common-vhdl-conversions>

Library IEEE: package NUMERIC_STD

Type conversion

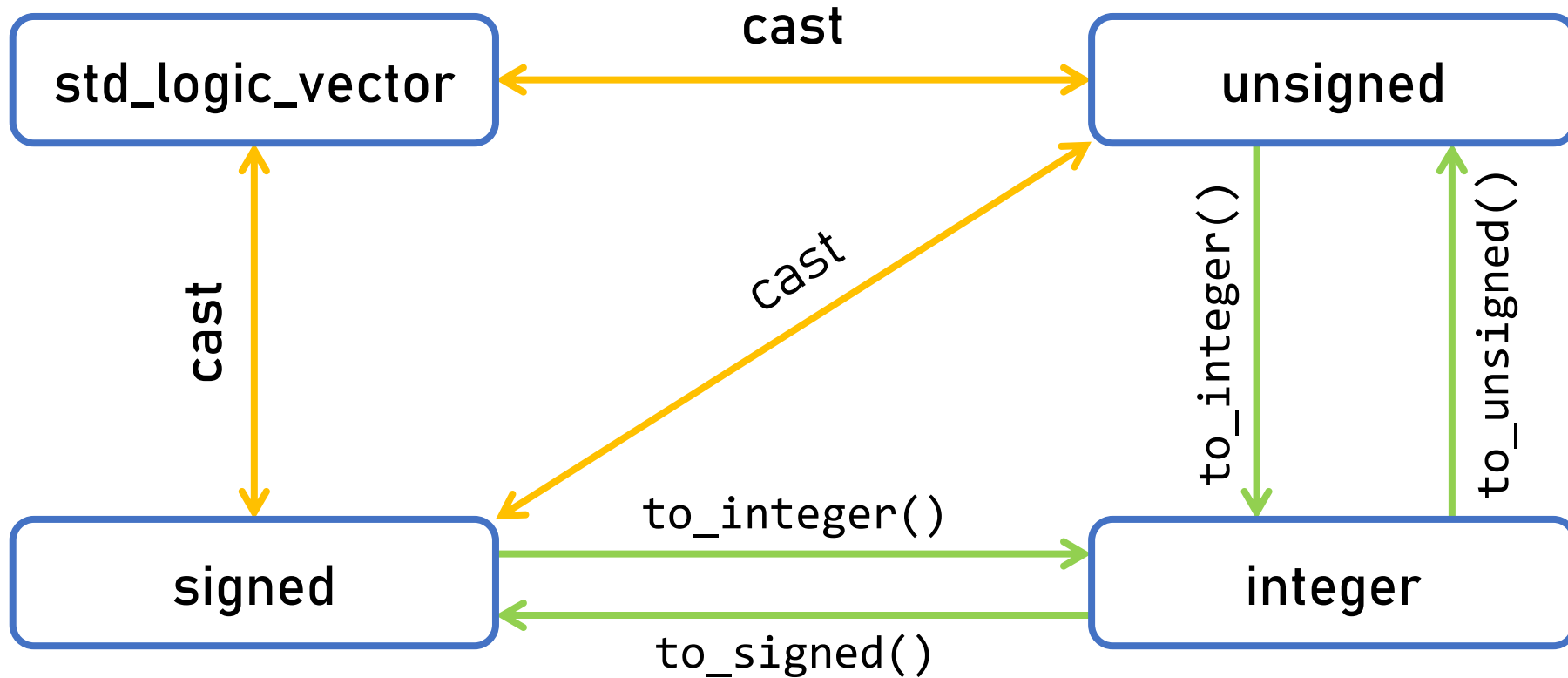

Challenge

Describe a module in VHDL that will generate the "scrolling LEDs" pattern:

- a block of four LEDs is scrolling (four LEDs are on)
- the first switch determines the direction of scrolling
 - when the switch is on, the direction of the scrolls is reversed (left to right)
- the second switch changes the scroll speed
 - when the switch is on, the pattern moves every 0.5 seconds, otherwise every 1 second
- the middle button (BNTC) resets the circuit