

# lab 03

## Generic modules, components, simulation

Digital design – laboratory exercises

assistant: Nejc Ilc

# Generalized modules - generic

- We use the generic clause to parameterize a module during the instantiation, e.g., n-bit counter.
- We specify a default value at declaration and the final value at instantiation.

```
entity counter is
port (
    clock: in  STD_LOGIC;
    reset: in  STD_LOGIC;
    value: out
           STD_LOGIC_VECTOR (3 downto 0);
);
end counter;
```

```
entity counter is
generic (n: integer := 8);
port (
    clock: in  STD_LOGIC;
    reset: in  STD_LOGIC;
    value: out
           STD_LOGIC_VECTOR (n-1 downto 0);
);
end counter;
```


# Components

- Our project should have a modular and clean structure.
- We want to reuse already built (generic) modules.
  - Example: we use the description of a n-bit counter for two counters: 4-bit and 8-bit.
- A concept of components enables us to instantiate and connect the already defined modules in a new module.

# Example

- Let's build a counter that will de/increment every second.
- We will split the design into three modules (files):
  - prescaler
    - inputs: clock, reset, limit
    - outputs: clock\_enable
  - counter
    - inputs : clock, reset, clock\_enable, count\_up, count\_down
    - outputs : value
  - top
    - connects the components prescaler and counter and defines the external interface

TOP

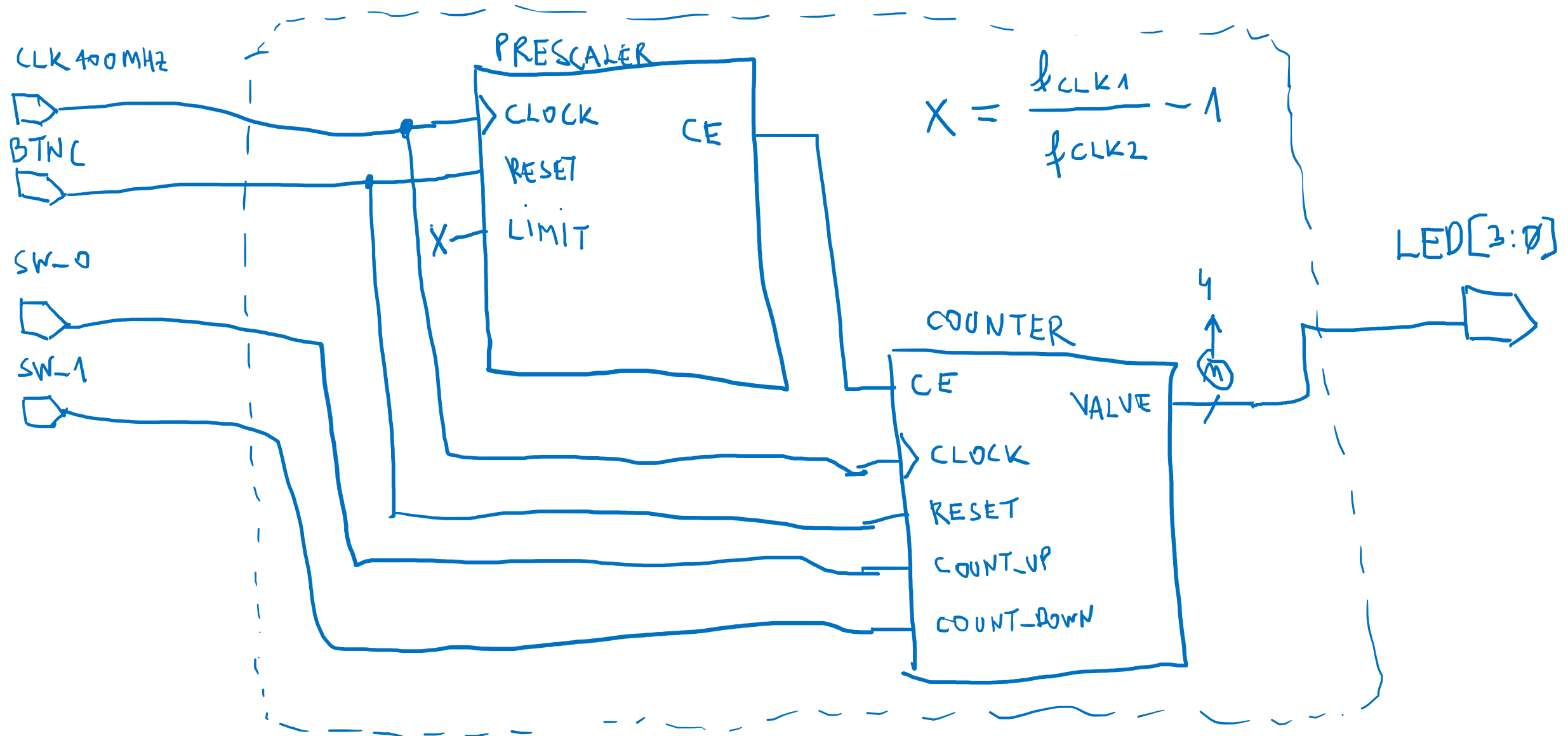

$$X = \frac{f_{CLK1}}{f_{CLK2}} - 1$$

# Module prescaler

```
entity prescaler is
  generic (
    width: integer := 8; -- the width of a prescaler counter
  );
  port (
    clock:          in  std_logic;
    reset:          in  std_logic;
    limit:          in  integer;
    clock_enable:  out  std_logic;
  );
end prescaler;
```

# Module counter

```
entity counter is
  generic (
    width: integer := 4;
  );
  port (
    clock:          in  std_logic;
    reset:          in  std_logic;
    clock_enable:   in  std_logic;
    count_up:       in  std_logic;
    count_down:     in  std_logic;
    value:          out signed(width-1 downto 0);
  );
end counter;
```

# Module top

- Top-most module cannot be generic.

```
entity top is
  port (
    CLK100MHZ: in  std_logic;
    BTNC:      in  std_logic;
    SW_0:      in  std_logic;
    SW_1:      in  std_logic;
    LED:       out signed(3 downto 0);
  );
end top;
```



# A wiring of components - port maps

- A component is a module that we use in the other module.
- Declaration (before begin in the architecture)

```
component component_name  
    port ( signal_name: direction type ...);  
end component;
```

- Port mapping

```
<label>: component_name  
port map (  
    signal_name_comp_1 => signal_name_top_1,  
    signal_name_comp_2 => signal_name_top_2,  
    ...  
);
```

# Example: declarations

```
-- Constants
constant f_clk_sys: integer := 100e6; -- 100 MHz
constant f_clk:    integer := 1; -- 1 Hz
constant cnt_width: integer := 4;
constant pr_width: integer := 27;
constant pr_limit: integer := f_clk_sys / f_clk - 1;

-- Internal signals
signal CE: std_logic := '0';
```

```
-- Components
component counter is generic (width: integer := 4);
    port (
        clock:        in  std_logic;
        reset :       in  std_logic;
        clock_enable: in  std_logic;
        count_up:     in  std_logic;
        count_down:   in  std_logic;
        value:        out signed (width-1 downto 0));
end component;

component prescaler is generic (width : integer := 27);
    port (
        clock:        in  std_logic;
        reset:        in  std_logic;
        limit:        in  integer;
        clock_enable: out std_logic);
end component;
```


# Example: instantiation

```
pr: prescaler
generic map (
  width => pr_width)
port map (
  clock          => CLK100MHZ,
  reset          => BTNC,
  clock_enable   => CE,
  limit          => pr_limit
);
```

```
cnt: counter
generic map (
  width => cnt_width)
port map (
  clock          => CLK100MHZ,
  reset          => BTNC,
  clock_enable   => CE,
  count_up       => SW_0,
  count_down     => SW_1,
  value          => LED
);
```
 
# Simulation

- We run "Behavioral simulation" before going into synthesis.
- Let's write a testing scenario, i.e., "test bench".
- We define stimuli of the module's inputs and observe its outputs.
- File → Add Sources ... → Add or Create Simulation Sources → Create File → <module\_name>\_tb.vhd



# Simulation: test bench

- Entity in a test bench does not have any inputs or outputs.
- In the architecture:
  - we declare and instantiate a component under test (UUT – unit under test),
  - we define stimuli using processes
    - a process for a clock,
    - a process for other stimuli.

# Simulation: test bench (2)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity top_tb is
end entity;

architecture Behavioral of top_tb is
    constant clock_period: time := 10 ns;
    signal clock:          std_logic := '0';
    signal reset:         std_logic := '0';
    signal count_up:      std_logic := '0';
    signal count_down:    std_logic := '0';
    signal counter_value: signed (3 downto 0);

    component top is
        port ( CLK100MHZ: in  std_logic;
              BTNC:      in  std_logic;
              SW_0:      in  std_logic;
              SW_1:      in  std_logic;
              LED:       out signed (3 downto 0));
    end component;

begin
    uut: top
        port map( CLK100MHZ => clock,
                 BTNC      => reset,
                 SW_0      => count_up,
                 SW_1      => count_down,
                 LED       => counter_value);
```



# Simulation: test bench (3)

```
clk: process
  begin
    wait for clock_period/2;
    clock <= not clock;
  end process;
```

```
stimuli: process
  begin
    reset <= '1';
    wait for 2*clock_period;
    reset <= '0';
    wait for 2*clock_period;
    count_up <= '1';
    wait for 15*clock_period;
    count_up <= '0';
    count_down <= '1';
    wait; -- wait forever ...
  end process;
end Behavioral;
```

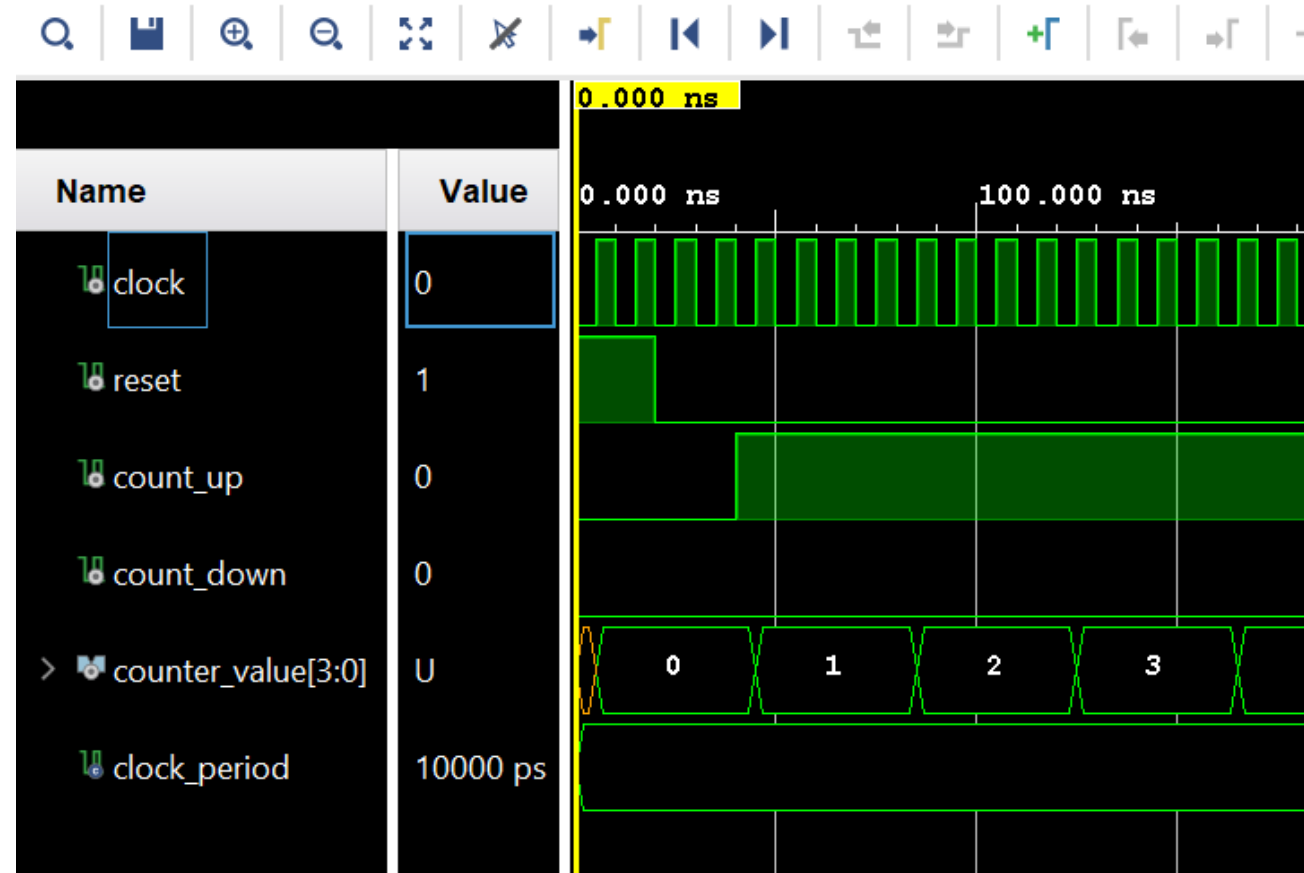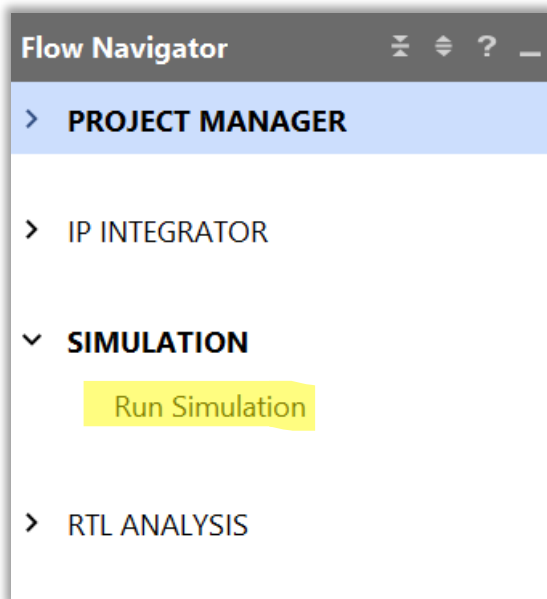
# Simulation: waveforms

- Launching a simulation:
  - Flow → Run Simulation → Run Behavioral Simulation





# Simulation: waveforms (2)

 

Note: the value of counter\_value is displayed as signed decimal number (Radix → Signed Decimal)

# Challenge

Solve the challenge 02 (a LED scroller) using components:

- `prescaler`
  - slows down the clock
  - let it have a generic width of a counter register
- `scroller`
  - it creates a scrolling effect on LEDs considering the prescaler "tempo"
  - let it have a generic width of a register that stores the state of LEDs; consequently, it means the number of LEDs we control.
- `top`
  - top module that wires the modules `prescaler` in `scroller` together.